

# Lecture 1


## Problems

➤ Derive the truth table and draw the logic circuits which correspond to the following expressions:

- a)  $F = A'BC' + A'BC + AB'$
- b)  $F = XY'Z + X'Y'Z + XYZ$
- c)  $F = [A(B+C') + A'B]C$
- d)  $F = XY'(Z+Y') + X'Z$
- e)  $F = (A+B').(A+B)'$

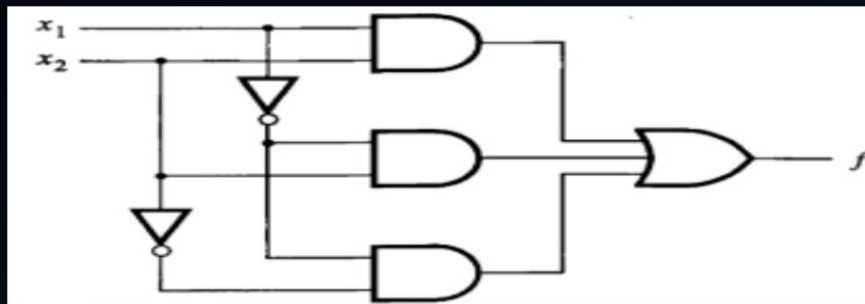
## Problems

➤ Which the logic expression corresponds to the following logical circuit:


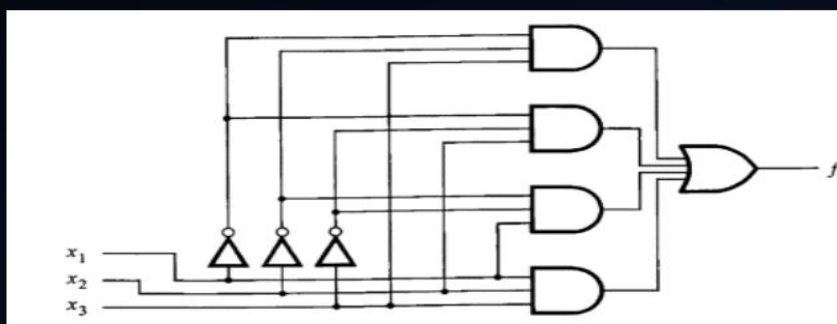
## Problems

➤ Which the logic expression corresponds to the following logical circuit and truth table:



# Lecture 2

## Exercises

➤ Draw the circuit to represent the following expressions: (By NAND gate only once and using NOR gate only once)

1.  $F = (x + y).z'$
2.  $F = (x' + y) . Z + w$
3.  $F = x.y.z + x.w'$

## Assignments

➤ Draw the NAND logic diagram for each of the following expressions:

1.  $F = (AB' + CD').E + BC (A + B)$
2.  $F = w.(x + y + z) + x.y.z$

# Lecture 3

## Assignment

□ Simplify the following Boolean expressions to a minimum number of literals:

1.  $XY + X(WZ + WZ')$
2.  $(BC' + A'D)(AB' + CD')$

□ Reduce the following Boolean expressions to the indicated number of literals:

1.  $A'C' + ABC + AC'$  to three literals
2.  $(X'Y' + Z') + Z + XY + WZ$  to three literals
3.  $A'B(D' + C'D) + B(A + A'CD)$
4.  $(A' + C)(A' + C')(A + B + C'D)$

# Lecture 4

## Assignments

- Find the complement of the following expressions:
  - $xy' + x'y$
  - $(x+y'+z)(x'+z')(x'+y)$
- Express the Boolean function in Sum of Minterms and Product of Maxterms:

$$F(A,B,C,D) = B'D + A'D + BD$$

## Assignments

- Find Sum of Product and Product of Sum to the functions of the following table

X	Y	Z	F1	F2	F3	F4
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0

# Lecture 5

## Assignments

➤ Simplify the following Boolean functions to a minimum number of literals:

- 1)  $A + AB$
- 2)  $AB + AB'$
- 3)  $X + X'Y$
- 4)  $(X + Y)(X + Y')$
- 5)  $A'BC + AC$
- 6)  $A'B + ABC' + ABC$
- 7)  $AB + A(CD + CD')$
- 8)  $XY + X'Z + YZ$
- 9)  $A'C' + AC' + ABC$
- 10)  $(BC' + A'D).(AB' + CD')$

## Assignments

➤ Answers to problems:

**3.1\*** Simplify the following Boolean functions, using three-variable maps:

(a)  $F(x, y, z) = \Sigma(0, 2, 6, 7)$

(b)  $F(x, y, z) = \Sigma(0, 2, 3, 4, 6)$

(c)  $F(x, y, z) = \Sigma(0, 1, 2, 3, 7)$

(d)  $F(x, y, z) = \Sigma(3, 5, 6, 7)$

**3.2** Simplify the following Boolean functions, using three-variable maps:

(a)\*  $F(x, y, z) = \Sigma(0, 1, 5, 7)$

(b)\*  $F(x, y, z) = \Sigma(1, 2, 3, 6, 7)$

(c)  $F(x, y, z) = \Sigma(0, 1, 6, 7)$

(d)  $F(x, y, z) = \Sigma(0, 1, 3, 4, 5)$

(e)  $F(x, y, z) = \Sigma(1, 3, 5, 7)$

(f)  $F(x, y, z) = \Sigma(1, 4, 5, 6, 7)$

**3.3\*** Simplify the following Boolean expressions, using three-variable maps:

(a)\*  $F(x, y, z) = xy + x'y'z' + x'yz'$

(b)\*  $F(x, y, z) = x'y' + yz + x'yz'$

(c)\*  $F(x, y, z) = x'y + yz' + y'z'$

(d)  $F(x, y, z) = xyz + x'y'z + xy'z'$

# Lecture 6

## Questions

- Draw the truth table of a three bits full adder. Use the output to draw the circuit diagram.
- Design a four-bit parallel subtractor circuit, then explain how you can use the circuit to subtract the following example  $1101-1011$ .



# Lecture 7

## Questions

- List with drawing the truth table of an 3x8 decoder circuit diagram
- List the truth table of an 3x8 decoder. Then draw the circuit diagram. Show how can you implement a full subtractor circuit using a 3x8 decoder.
- Construct 3x8 decoder using 2x4 decoders, then write the truth table.
- Construct 4x16 decoder using 3x8 decoders